

# **CSM152A-LAB 4**

Lab 5

Yichen Lyu

UID: 004940413

May 24, 2020

## 1. INTRODUCTION

This lab will explore how to design, implement and test using Xilinx a finite state machine (FSM). The FSM this lab will use is a mealy machine, whose output depends on both its input and state. The final project should be a vending machine with 20 snacks. Each snack has a price and a number left. If a card is detected, the transaction process starts and only one item can be purchased at the same time.

## 2. DESIGN DESCRIPTION

The overall FSM will have two internal arrays: `COSTS[]` and `counts[]`. `COSTS[]` is a constant array that stores the price of an item based on its item code. `counts[]` contains the number of items left based on item code. There is also a 5-bit counter, `cycle_count`, which counts the number of cycles that the FSM has been waiting in one state. The current state and the next state are recorded in `vend_state` and `nx_vend_state`. Every time there is a posedge `clk`, `vend_state` will be given the value of `nx_vend_state`. The input and output signals are shown below.

The overall design of the FSM is given in the graph below.

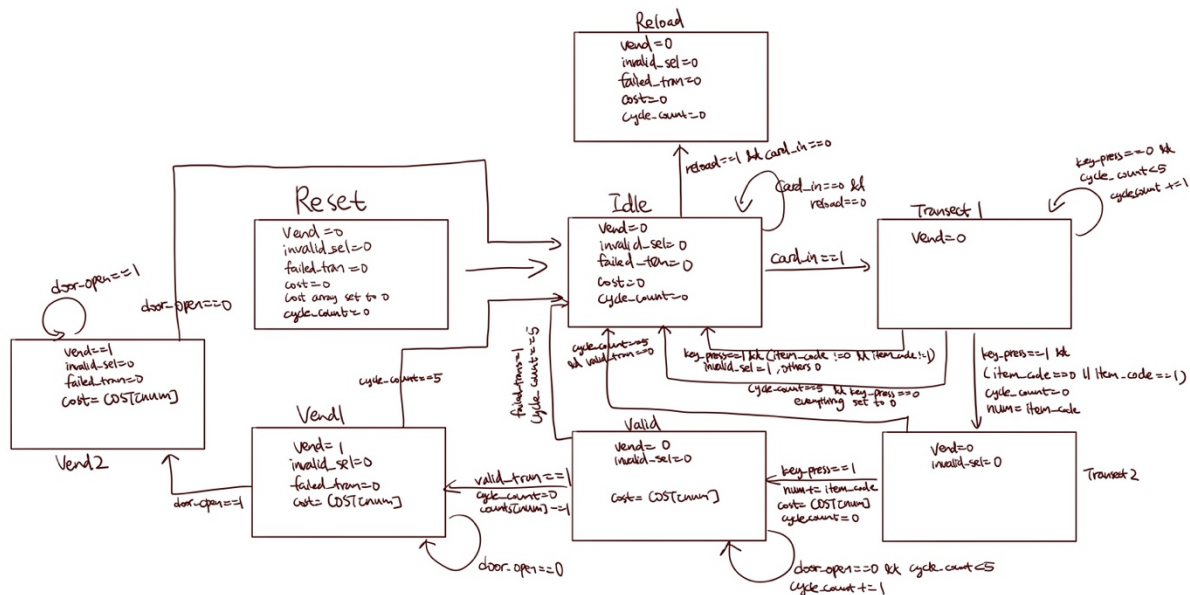


Figure 1: Overall Combinational Circuit Design

The FSM is implemented using a case statement using `vend_state`. Within each case, if statements are used to assign outputs based on inputs.

## 2.1 RESET

1. When rst is 1, vend\_state will be set to RESET.
2. The program enters case RESET and sets every output to 0 and counts[] to be 0 with a for loop.
3. If rst == 0, nx\_vend\_state is set to IDLE. Otherwise, it loops in RESET.

## 2.2 IDLE

1. All outputs are set to 0.
2. If card\_in is 1, IDLE's next state is set to TRANSECT1.
3. If card\_in is 0, but reload is 1, it sets nx\_vend\_state to RELOAD.
4. Otherwise, it keeps looping back to IDLE, as indicated in the design.

## 2.3 RELOAD

1. All outputs are 0, but it does not have to intentionally set any output because it can only come after IDLE, who has already set every output to 0.
2. It sets all product counts to 10. (It is implemented by setting counts[] to 10 using a for loop).
3. It always sets its next state to IDLE.

## 2.4 TRANSECT1

1. This state waits for the first digit of item code.
2. If key\_press and card\_in are both 1, it takes in the value in item\_code and check if it is valid as a first digit of the overall item code. For the first digit, the value in item\_code can only be 0 or 1. If it is not valid, invalid\_sel is set high and nx\_vend\_state is IDLE.
3. If item\_code is valid, nx\_vend\_state is TRANSECT2.
4. If key\_press is not high after 5 clock cycles, we set nx\_vend\_state to IDLE. (The cycle count is stored in cycle\_count, which counts up to 9. This is because the always loop the case statement is in is triggered both on posedge and negedge. cycle\_count is increased by 2 each cycle. Thus, we double the cycle count from 5 to 9)

## 2.5 TRANSECT2

1. This state waits for the second digit.
2. Every value will be valid as a second digit, so invalid\_sel is always 0.
3. If key\_press becomes high, it calculates the overall item code. It sets cost using the corresponding price of the item code. nx\_vend\_state is VALID.
4. As long as key\_press is low, we loop in TRANSECT2.
5. If key\_press does not become high in 5 cycles, nx\_vend\_state is set to IDLE.

(it adds the second item\_code to 10\*first\_item\_code, whose value is stored in a register num. cost will be set to the value of COST[num]). nx\_vend\_state will be set to VALID. As long as key\_press is low, we loop in TRANSECT2. If key\_press does not become high in 5 cycles (using the same counting way in TRANSECT1), nx\_vend\_state is set to IDLE.

## 2.6 VALID

1. This state waits for valid\_tran to become high.
2. If valid\_tran is high, this transaction is validated and we can start vending: it sets nx\_vend\_state to VEND1.
3. If valid\_tran is low, it keeps looping to itself up to 5 cycles.
4. If valid\_tran does not go high in 5 cycles, the transaction fails. Failed\_tran is set high and nx\_vend\_state becomes IDLE.

After the 2 digits are received, num is set to the correct value of the overall item code. So in VALID, cost is still COST[num].


## 2.6 VEND1

1. The machine starts vending. Vend is set high, and VEND1 waits for door\_open to be 1.
2. If door\_open is high, its nx\_vend\_state becomes VEND2.
3. If door\_open is low, it loops back to itself for up to 5 cycles.
4. After waiting for 5 cycles, nx\_vend\_state is set to IDLE.

## 2.6 VEND2

1. The machine waits for door to close. Once door\_open becomes low again, it goes back to IDLE.
2. If door\_open does not become low, it keeps looping to VEND2.

## 3. SCHEMATICS

 

 


Figure 2: Auto Generated Schematics

The generated schematics is very complex. The next state is constantly influenced by the input, so we need flip-flops to combine inputs and the clock signal to determine the next state, which is fed back into the circuit to become the current state for the next round. We also need many MUXes because the outputs are based on many if-statements, depending on the state and the input.

## 4. SIMULATION

### 4.1 Complete Transection

In a complete transection, the FSM first detects reload and enters RELOAD(0010). There, it changes all item stocks to be 10, and all outputs remain 0. It then falls back to IDLE(0001). Then, it detects card\_in and enters TRANSECT1(0011) from IDLE. It sees that key\_press is high, so it takes in item\_code, which is 1. Since 1 is valid as a first digit, it goes to TRANSECT2(0100). There, it waits for a cycle for key\_press is high and takes in item\_code, which is 4. It calculates the overall item code ( $1 \times 10 + 4 = 14$ ) and accordingly sets cost to 4. It then enters the next state, VALID(0111) where it sees that valid\_tran is high. Thus, it goes to VEND1(0101) and sets vend to 1. Other outputs remain the same as the previous state. It detects that door\_open is high, so it goes to VEND2(0110), where it sees that door\_open becomes low again. It then completes the whole cycle by going back to IDLE.

 


Figure 3: Successful Transection (need to change vend!)

### 4.2 Timeout on First Item Code

In this case, key\_press is not set high after the FSM detects card\_in and enters TRANSECT1 (0011) from IDLE (0000). Vend\_state loops in TRANSECT1 for 5 cycles and then goes to IDLE. During this process, all outputs remain 0.

 


Figure 4: TRANSECT1 Timeout

### 4.3 Invalid Item Code

In this case, the FSM enters TRANSECT1(0011) and receives a high key\_press. It then takes in the value in item\_code, which is 4. The first digit can only be 0 or 1, so it knows that this digit is invalid. It then sets invalid\_sel to be high and go back to IDLE(0001). In the simulation below, card\_in and key\_press are not set low, so after it enters IDLE, it keeps going back to TRANSECT1 and takes in the invalid code 4, so invalid\_sel is constantly set high.

 


Figure 5: invalid\_sel

### 4.4 Timeout on Second Item Code

In this case, the FSM enters TRANSECT1(0011) from IDLE(0001). It detects key\_press to be high and reads in the item code (0001). It determines that 1 is a valid first digit and goes to TRANSECT2(0100). Now, key\_press is low, so it waits for it to become high. After 5 cycles, it times out and goes back to IDLE.

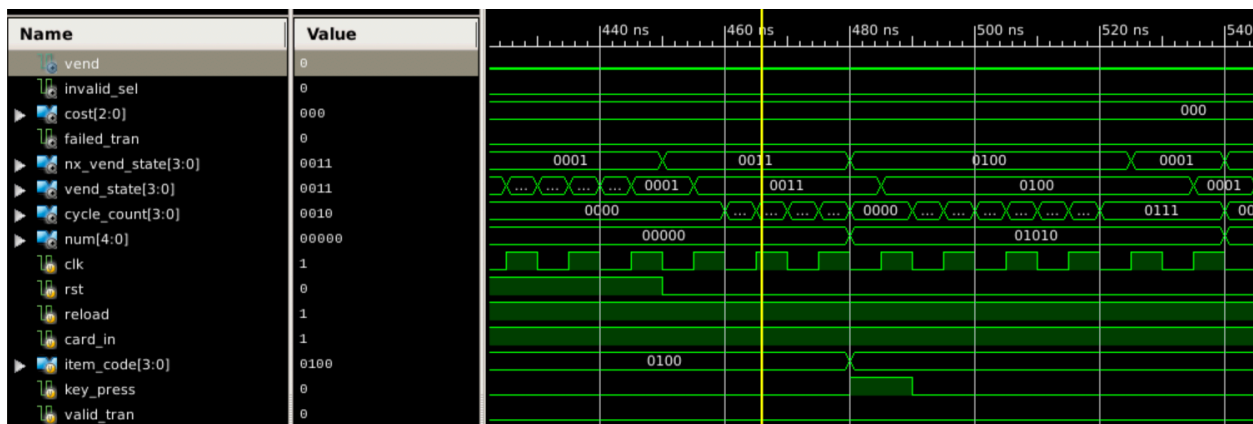


Figure 6: TRANSECT2 Timeout

4.5 Timeout on VALID\_TRAN

In this case, the FSM receives high key\_press within 5 cycles in TRANSECT2(0100) and enters VALID(0111). Both item codes are 1, so the overall code is 11, and the cost is 3. It waits for valid\_tran to be high until timeout. In the fifth cycle, when it detects valid\_tran is still low, it sets failed\_tran to be 1. Then it enters IDLE(0001), where every output is set to 0 again.

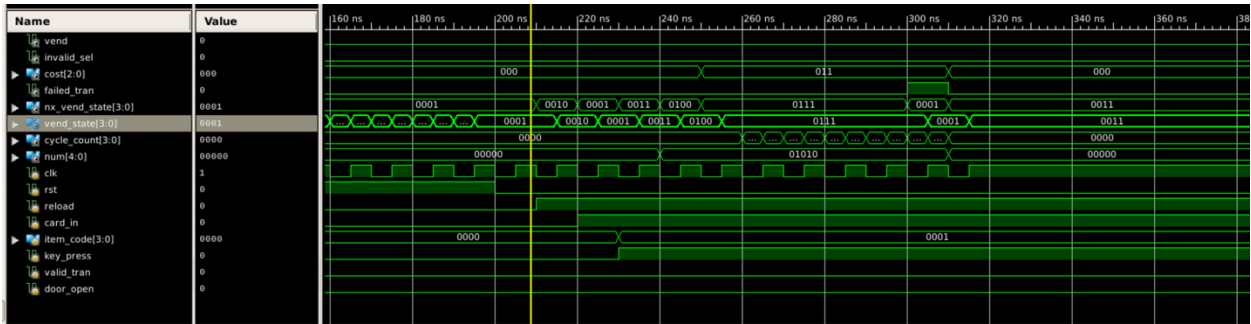


Figure 7: VALID Timeout

4.6 Timeout on DOOR\_OPEN

In this case, after receiving high valid\_trans in VALID (0111), the FSM enters VEND1 (0101). It waits for door\_open to be 1. After 5 cycles, it times out and goes back to IDLE(0001). The cost remains the same ever since TRANSECT2(0100), which inputs item code 14 and gets the output as 4. Vend is set. Other outputs are low.

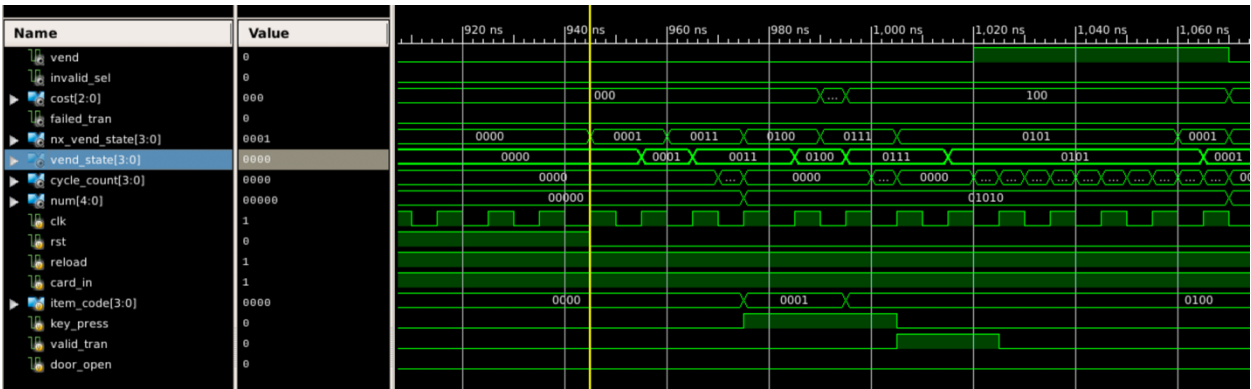


Figure 8: VEND1 Timeout (need change)



#### 4.7 Door Does Not Close

In this case, the door opens in VEND1(0101), so the FSM enters VEND2(0110). Here, it waits for door\_open to become 0. As door\_open is never set low again, it loops in VEND2 forever. The cost remains the same ever since TRANSECT2(0100), which inputs item code 11 and gets the output as 3. Vend is set high in VEND1 and remains high here. Other outputs are low.

 


Figure 9: VEND2 Timeout (need change!)

#### 5. CONCLUSION

This lab allows us to explore how to build a finite state machine using case statement in Xilinx ISE. It helps us learn how to divide a real-life problem into different states of the FSM and implement it with if statements to determine the outputs and the following state. Cooperating between input and state assignment is the key for the implementation of a mealy machine.

## 6. APPENDIX: DESIGN SUMMARY REPORT

### 6.1 Design Summary

vending_machine Project Status (05/21/2020 - 21:19:34)			
<b>Project File:</b>	lab4.xise	<b>Parser Errors:</b>	No Errors
<b>Module Name:</b>	vending_machine	<b>Implementation State:</b>	Placed and Routed
<b>Target Device:</b>	xc6slx16-3csg324	• <b>Errors:</b>	No Errors
<b>Product Version:</b>	ISE 14.7	• <b>Warnings:</b>	<a href="#">55 Warnings (13 new)</a>
<b>Design Goal:</b>	Balanced	• <b>Routing Results:</b>	<a href="#">All Signals Completely Routed</a>
<b>Design Strategy:</b>	<a href="#">Xilinx Default (unlocked)</a>	• <b>Timing Constraints:</b>	<a href="#">All Constraints Met</a>
<b>Environment:</b>	<a href="#">System Settings</a>	• <b>Final Timing Score:</b>	0 ( <a href="#">Timing Report</a> )

Device Utilization Summary					<a href="#">[-]</a>
Slice Logic Utilization	Used	Available	Utilization	Note(s)	
Number of Slice Registers	9	18,224	1%		
Number used as Flip Flops	4				
Number used as Latches	5				
Number used as Latch-thrus	0				
Number used as AND/OR logics	0				
Number of Slice LUTs	27	9,112	1%		
Number used as logic	27	9,112	1%		
Number using O6 output only	18				
Number using O5 output only	0				
Number using O5 and O6	9				
Number used as ROM	0				
Number used as Memory	0	2,176	0%		
Number of occupied Slices	11	2,278	1%		
Number of MUXCYs used	0	4,556	0%		
Number of LUT Flip Flop pairs used	28				
Number with an unused Flip Flop	19	28	67%		
Number with an unused LUT	1	28	3%		
Number of fully used LUT-FF pairs	8	28	28%		
Number of unique control sets	3				
Number of slice register sites lost to control set restrictions	15	18,224	1%		
Number of bonded <a href="#">IOBs</a>	34	232	14%		
IOB Latches	8				
Number of RAMB16BWERS	0	32	0%		
Number of RAMB8BWERS	0	64	0%		
Number of BUFIO2/BUFIO2_2CLKs	0	32	0%		
Number of BUFIO2FB/BUFIO2FB_2CLKs	0	32	0%		
Number of BUFG/BUFGMUXs	1	16	6%		
Number used as BUFGs	1				
Number used as BUFGMUX	0				
Number of DCM/DCM_CLKGENs	0	4	0%		
Number of ILOGIC2/ISERDES2s	0	248	0%		
Number of IODELAY2/IODRP2/IODRP2_MCBs	0	248	0%		
Number of OLOGIC2/OSERDES2s	8	248	3%		
Number used as OLOGIC2s	8				
Number used as OSERDES2s	0				
Number of BSCANs	0	4	0%		
Number of BUFHs	0	128	0%		
Number of BUFPLLs	0	8	0%		
Number of BUFPLL_MCBs	0	4	0%		
Number of DSP48A1s	0	32	0%		
Number of ICAPs	0	1	0%		
Number of MCBs	0	2	0%		
Number of PCILOGICSEs	0	2	0%		
Number of PLL_ADVs	0	2	0%		
Number of PMVs	0	1	0%		

Number of PCILOGICSEs	0	2	0%	
Number of PLL_ADVs	0	2	0%	
Number of PMVs	0	1	0%	
Number of STARTUPs	0	1	0%	
Number of SUSPEND_SYNCs	0	1	0%	
Average Fanout of Non-Clock Nets	3.42			

Performance Summary				<a href="#">[-]</a>
<b>Final Timing Score:</b>	0 (Setup: 0, Hold: 0)		<b>Pinout Data:</b>	<a href="#">Pinout Report</a>
<b>Routing Results:</b>	<a href="#">All Signals Completely Routed</a>		<b>Clock Data:</b>	<a href="#">Clock Report</a>
<b>Timing Constraints:</b>	<a href="#">All Constraints Met</a>			

Detailed Reports						<a href="#">[-]</a>
Report Name	Status	Generated	Errors	Warnings	Infos	
<a href="#">Synthesis Report</a>	Current	Thu May 21 21:29:34 2020	0	<a href="#">49 Warnings (7 new)</a>	<a href="#">3 Infos (1 new)</a>	
<a href="#">Translation Report</a>	Current	Thu May 21 21:29:42 2020	0	0	0	
<a href="#">Map Report</a>	Current	Thu May 21 21:29:54 2020	0	<a href="#">6 Warnings (6 new)</a>	<a href="#">6 Infos (0 new)</a>	
<a href="#">Place and Route Report</a>	Current	Thu May 21 21:30:03 2020	0	0	<a href="#">3 Infos (0 new)</a>	
Power Report						
<a href="#">Post-PAR Static Timing Report</a>	Current	Thu May 21 21:30:09 2020	0	0	<a href="#">4 Infos (0 new)</a>	
Bitgen Report						

Secondary Reports			<a href="#">[-]</a>
Report Name	Status	Generated	
<a href="#">ISIM Simulator Log</a>	Out of Date	Thu May 21 21:27:41 2020	

Date Generated: 05/21/2020 - 21:19:34

## 6.2 Implementation Design Summary

```
=====
*                               Design Summary                               *
=====

Top Level Output File Name      : vending_machine.ngc

Primitive and Black Box Usage:
-----
# BELS                          : 51
#   LUT2                        : 4
#   LUT3                        : 7
#   LUT4                        : 5
#   LUT5                        : 13
#   LUT6                        : 20
#   MUXF7                       : 2
# FlipFlops/Latches             : 18
#   FDC                         : 3
#   LD                          : 15
# Clock Buffers                 : 1
#   BUFG                        : 1
# IO Buffers                    : 17
#   IBUF                       : 11
#   OBUF                       : 6

Device utilization summary:
-----

Selected Device : 6slx16csg324-3

Slice Logic Utilization:
Number of Slice Registers:      12 out of 18224    0%
Number of Slice LUTs:          49 out of 9112     0%
Number used as Logic:          49 out of 9112     0%

Slice Logic Distribution:
Number of LUT Flip Flop pairs used: 49
Number with an unused Flip Flop: 37 out of 49    75%
Number with an unused LUT:        0 out of 49    0%
Number of fully used LUT-FF pairs: 12 out of 49   24%
Number of unique control sets:    7

IO Utilization:
Number of IOs:                  17
Number of IOs:                  17
Number of bonded IOBs:          17 out of 232    7%
IOB Flip Flops/Latches:         6

Specific Feature Utilization:
Number of BUFG/BUFGCTRLs:       1 out of 16      6%

-----
Partition Resource Summary:
-----

No Partitions were found in this design.

-----
=====
```

## 6.3 Map Summary

Design Summary				
-----				
Number of errors:	0			
Number of warnings:	6			
Slice Logic Utilization:				
Number of Slice Registers:	12 out of	18,224	1%	
Number used as Flip Flops:	3			
Number used as Latches:	9			
Number used as Latch-thrus:	0			
Number used as AND/OR logics:	0			
Number of Slice LUTs:	36 out of	9,112	1%	
Number used as logic:	36 out of	9,112	1%	
Number using 06 output only:	23			
Number using 05 output only:	0			
Number using 05 and 06:	13			
Number used as ROM:	0			
Number used as Memory:	0 out of	2,176	0%	
Slice Logic Distribution:				
Number of occupied Slices:	12 out of	2,278	1%	
Number of MUXCYs used:	0 out of	4,556	0%	
Number of LUT Flip Flop pairs used:	37			
Number with an unused Flip Flop:	25 out of	37	67%	
Number with an unused LUT:	1 out of	37	2%	
Number of fully used LUT-FF pairs:	11 out of	37	29%	
Number of unique control sets:	3			
Number of slice register sites lost to control set restrictions:	12 out of	18,224	1%	
A LUT Flip Flop pair for this architecture represents one LUT paired with one Flip Flop within a slice. A control set is a unique combination of clock, reset, set, and enable signals for a registered element. The Slice Logic Distribution report is not meaningful if the design is over-mapped for a non-slice resource or if Placement fails.				
IO Utilization:				
Number of bonded IOBs:	17 out of	232	7%	
IOB Latches:	6			
Specific Feature Utilization:				
Number of RAMB16BWRs:	0 out of	32	0%	
Number of RAMB8BWRs:	0 out of	64	0%	
Number of BUFI02/BUFI02_2CLKs:	0 out of	32	0%	
Number of BUFI02FB/BUFI02FB_2CLKs:	0 out of	32	0%	
Number of RAMB16BWRs:	0 out of	32	0%	
Number of RAMB8BWRs:	0 out of	64	0%	
Number of BUFI02/BUFI02_2CLKs:	0 out of	32	0%	
Number of BUFI02FB/BUFI02FB_2CLKs:	0 out of	32	0%	
Number of BUFG/BUFGMUXs:	1 out of	16	6%	
Number used as BUFGs:	1			
Number used as BUFGMUX:	0			
Number of DCM/DCM_CLKGENs:	0 out of	4	0%	
Number of ILOGIC2/ISERDES2s:	0 out of	248	0%	
Number of IODELAY2/IODRP2/IODRP2_MCBs:	0 out of	248	0%	
Number of OLOGIC2/OSERDES2s:	6 out of	248	2%	
Number used as OLOGIC2s:	6			
Number used as OSERDES2s:	0			
Number of BSCANs:	0 out of	4	0%	
Number of BUFHs:	0 out of	128	0%	
Number of BUFPLLs:	0 out of	8	0%	
Number of BUFPLL_MCBs:	0 out of	4	0%	
Number of DSP48A1s:	0 out of	32	0%	
Number of ICAPs:	0 out of	1	0%	
Number of MCBs:	0 out of	2	0%	
Number of PCILOGICSEs:	0 out of	2	0%	
Number of PLL_ADVs:	0 out of	2	0%	
Number of PHVs:	0 out of	1	0%	
Number of STARTUPs:	0 out of	1	0%	
Number of SUSPEND_SYNCs:	0 out of	1	0%	

Comment: The implementation requires a lot of flip-flops because they are important for the realization of state assignment for each clock cycle.